

1. Derivation of State Graphs and Tables

(1) Designate the circuit states


S_0 — a reset state, If a 0 input is received.

S_1 — a 1 is received.

S_2 — 11 is received.


S_3 — 110 is received, and the output $Z=1$.

(2) Analyze transition of the states

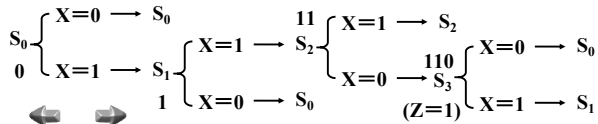

Sequential Circuits Design

(3) State Graphs

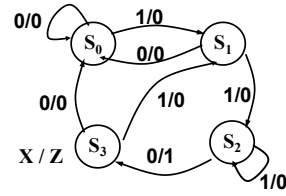

(4) State Tables

$Y_n X$	Y_{n+1} / Z	
	0	1
S_0	$S_0 / 0$	$S_1 / 0$
S_1	$S_0 / 0$	$S_2 / 0$
S_2	$S_3 / 1$	$S_2 / 0$
S_3	$S_0 / 0$	$S_1 / 0$

2. Reduction of State Tables.

$Y_n X$	Y_{n+1} / Z	
	0	1
S_0	$S_0 / 0$	$S_1 / 0$
S_1	$S_0 / 0$	$S_2 / 0$
S_2	$S_3 / 1$	$S_2 / 0$
S_3	$S_0 / 0$	$S_1 / 0$

$Y_n X$	Y_{n+1} / Z	
	0	1
S_0	$S_0 / 0$	$S_1 / 0$
S_1	$S_0 / 0$	$S_2 / 0$
S_2	$S_0 / 1$	$S_2 / 0$

3. State Assignment


Use 2 flip-flops

$y_2 y_1$

S_0 — 00


S_1 — 10

S_2 — 11

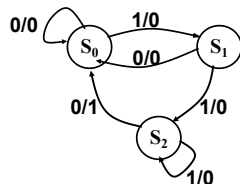

Sequential Circuits Design

4. Form the transition table

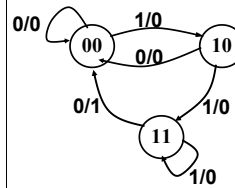

$X Y_2 Y_1$	$Y_2^{n+1} Y_1^{n+1}$	$J_2 K_2$	$J_1 K_1$	Z
0 0 0	0 0	0 × 0 ×	0 × 0 ×	0
0 1 1	0 0	× 1 × 1	× 1 × 1	1
0 1 0	0 0	× 1 0 ×	× 1 0 ×	0
1 0 0	1 0	1 × 0 ×	1 × 0 ×	0
1 1 1	1 1	× 0 × 0	× 0 × 0	0
1 1 0	1 1	× 0 1 ×	× 0 1 ×	0
0 0 1	× ×	× × × ×	× × × ×	×
1 0 1	× ×	× × × ×	× × × ×	×

5. Derive the flip-flop input equations and the output functions using K. maps.

J_2 K-map:

$Y_2 Y_1$	00	01	11	10
0	0	×	×	×
1	1	×	×	×

$J_2 = X$

K_2 K-map:

$Y_2 Y_1$	00	01	11	10
0	×	×	1	1
1	×	×	0	0

$K_2 = \bar{X}$

$X Y_2 Y_1$	$Y_2^{n+1} Y_1^{n+1}$	$J_2 K_2$	$J_1 K_1$	Z
0 0 0	0 0	0 × 0 ×	0 × 0 ×	0
0 1 1	0 0	× 1 × 1	× 1 × 1	1
0 1 0	0 0	× 1 0 ×	× 1 0 ×	0
1 0 0	1 0	1 × 0 ×	1 × 0 ×	0
1 1 1	1 1	× 0 × 0	× 0 × 0	0
1 1 0	1 1	× 0 1 ×	× 0 1 ×	0
0 0 1	× ×	× × × ×	× × × ×	×
1 0 1	× ×	× × × ×	× × × ×	×

J_1 K-map:

$Y_2 Y_1$	00	01	11	10
0	0	×	×	×
1	0	×	×	1

$J_1 = X Y_2$

K_1 K-map:

$Y_2 Y_1$	00	01	11	10
0	×	×	1	×
1	×	×	0	×

$K_1 = \bar{X}$


Z K-map:

$Y_2 Y_1$	00	01	11	10
0	0	×	1	0
1	0	×	0	0

$Z = \bar{X} Y_1$

$X Y_2 Y_1$	$Y_2^{n+1} Y_1^{n+1}$	$J_2 K_2$	$J_1 K_1$	Z
0 0 0	0 0	0 × 0 ×	0 × 0 ×	0
0 1 1	0 0	× 1 × 1	× 1 × 1	1
0 1 0	0 0	× 1 0 ×	× 1 0 ×	0
1 0 0	1 0	1 × 0 ×	1 × 0 ×	0
1 1 1	1 1	× 0 × 0	× 0 × 0	0
1 1 0	1 1	× 0 1 ×	× 0 1 ×	0
0 0 1	× ×	× × × ×	× × × ×	×
1 0 1	× ×	× × × ×	× × × ×	×

6. Realize the circuit

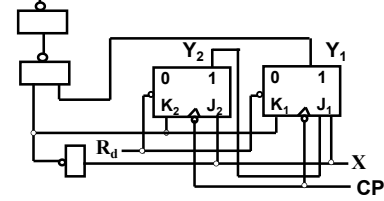


7. Check all the don't-care states

$$Y_1^{n+1} = XY_2\bar{Y}_1 + XY_1$$

$$= X(Y_1 + Y_2)$$

$$Y_2^{n+1} = X\bar{Y}_2 + XY_2$$


$$= X$$

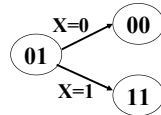


1. Derivation of State Graphs and Tables

Analyze

1. Reusable:

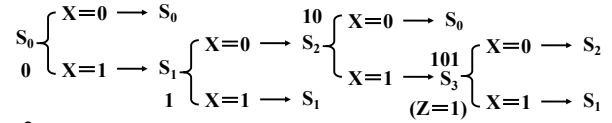

2. Nonreusable:

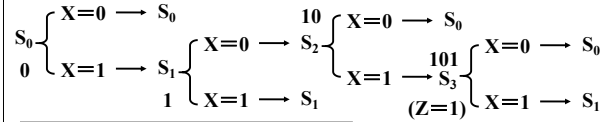


States:

S_0 —0, S_1 —1

S_2 —10, S_3 —101, and $Z=1$



Nonreusable

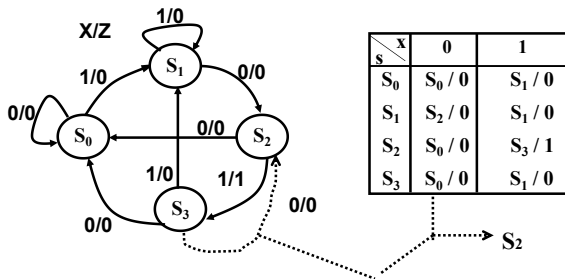

States:

S_0 —0, S_1 —1

S_2 —10, S_3 —101, and $Z=1$

reusable




Beverage vending machines

- Accept coins only: 0.5¥, 1¥
- Accept only one coin each time
- If 1.5 ¥ coins are inserted into the slot, you will get a bottle of drink
- If 2.0 ¥ coins are inserted into the slot, you will get a bottle of drink and 0.5¥ change



Beverage vending machines

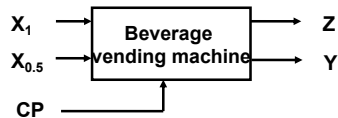

$X_1 = 1$: insert a coin (1¥)

$X_1 = 0$: don't insert a coin (1¥)

$X_{0.5} = 1$: insert a coin (0.5¥)

$X_{0.5} = 0$: don't insert a coin (0.5¥)

$Y=1$: get a bottle of drink

$Y=0$: don't get a bottle of drink

$Z=1$: get a change (0.5 ¥ coin)

$Z=0$: don't get a change (0.5 ¥ coin)

Beverage vending machines

1. Derivation of State Graphs and Tables

① Designate the circuit states

S_0 —a reset state, no coin is inserted.

S_1 —0.5 ¥ is received.

S_2 —1.0 ¥ is received (2 coins of 0.5 ¥, or a coin of 1.0 ¥)

If a 0.5 ¥ coin is inserted,

then $Y=1$, $Z=0$, state go to S_0


Else If a 1.0 ¥ coin is inserted,

then $Y=1$, $Z=1$, and state go to S_0


Solution 1:

Mealy circuit

② Analyze

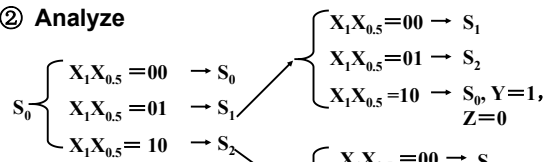

③ Mealy State Graph

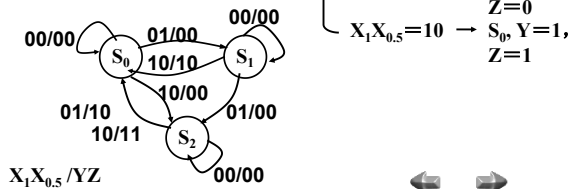

④ State Table

	S_{n+1} / YZ			
$X_1 X_{0.5}$	00	01	10	11
S_0	$S_0 / 00$	$S_1 / 00$	$S_2 / 00$	$\times / \times \times$
S_1	$S_1 / 00$	$S_2 / 00$	$S_0 / 10$	$\times / \times \times$
S_2	$S_2 / 00$	$S_0 / 10$	$S_0 / 11$	$\times / \times \times$

2. Reduction of State Table

3. State Assignment

$S_0 \text{ — } 00$
 $S_1 \text{ — } 01$
 $S_2 \text{ — } 10$

$\because N=3, 2^2 > 3$
 $\therefore k=2$
 Need 2 flip flops

4. transition table

$X_1 X_{0.5}$	$Q_1 Q_2$	$Q_1^{n+1} Q_2^{n+1}$	$Y Z$	$D_1 D_2$
00	00	00	00	00
00	01	01	00	01
00	10	10	00	10
00	11	$\times \times$	$\times \times$	$\times \times$
01	00	01	00	01
01	01	10	00	10
01	10	00	10	00
01	11	$\times \times$	$\times \times$	$\times \times$
10	00	10	00	10
10	01	00	10	00
10	10	00	11	00
10	11	$\times \times$	$\times \times$	$\times \times$
11	00	$\times \times$	$\times \times$	$\times \times$
11	01	$\times \times$	$\times \times$	$\times \times$
11	10	$\times \times$	$\times \times$	$\times \times$
11	11	$\times \times$	$\times \times$	$\times \times$

5. K.maps

D_1

$Q_1 Q_2$	00	01	11	10
$X_1 X_{0.5}$	0	0	\times	1
00	0	1	\times	0
01	\times	\times	\times	\times
11	1	0	\times	0

D_2

$Q_1 Q_2$	00	01	11	10
$X_1 X_{0.5}$	0	1	\times	0
00	1	0	\times	\times
01	\times	\times	\times	\times
11	0	0	\times	0

$$D_1 = \bar{X}_1 \bar{X}_{0.5} Q_1 + Q_2 X_{0.5} + X_1 \bar{Q}_1 \bar{Q}_2$$

$$D_2 = \bar{X}_1 \bar{X}_{0.5} Q_1 + X_{0.5} \bar{Q}_1 \bar{Q}_2$$

Y

$Q_1 Q_2$	00	01	11	10
$X_1 X_{0.5}$	0	0	\times	0
00	0	0	\times	1
01	\times	\times	\times	\times
11	0	1	\times	1


$$Y = X_1 X_{0.5} + Q_2 X_1 + X_1 Q_1$$

Z

$Q_1 Q_2$	00	01	11	10
$X_1 X_{0.5}$	0	0	\times	0
00	0	0	\times	0
01	\times	\times	\times	\times
11	0	0	\times	1


$$Z = X_1 Q_1$$

6. Realize

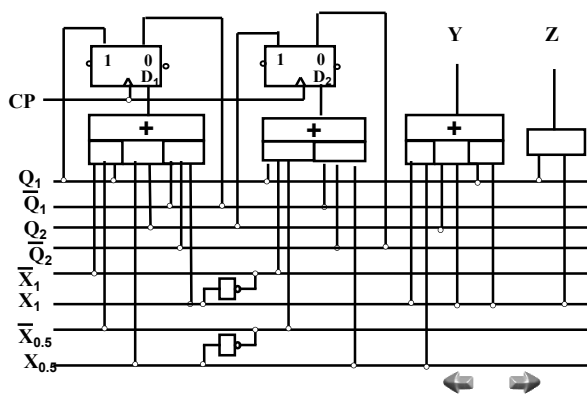

7. Recheck

Don't care state $Q_1 Q_2 = 11$

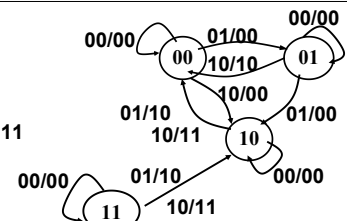

$X_1 X_{0.5} = 00 :$

$$\begin{aligned} Q_1^{n+1} &= D_1 = \bar{X}_1 \bar{X}_{0.5} Q_1 + Q_2 X_{0.5} + X_1 \bar{Q}_1 \bar{Q}_2 \\ Q_2^{n+1} &= D_2 = \bar{X}_1 \bar{X}_{0.5} Q_2 + X_{0.5} \bar{Q}_1 \bar{Q}_2 \end{aligned} \rightarrow 11 \text{ Non-Self-Starting}$$

$X_1 X_{0.5} = 01 (10) : \rightarrow 10 \text{ Self-Starting, but error in charging}$

! Reset circuit with R_D at beginning

Moor Circuit

Solution 2:


- **Output:** $Z_1=1 \rightarrow$ get a bottle of drink, $Z_2=1 \rightarrow$ change
all possible output $Z_1Z_2 = 00, 10, 11$
- **Input:** $X_1X_2 = 00 \rightarrow 0 \text{ ¥};$
 $X_1X_2 = 01 \rightarrow 0.5 \text{ ¥};$
 $X_1X_2 = 10 \rightarrow 1.0 \text{ ¥}.$
- **State:** remember the money received

$S_0 = 0 \text{ ¥}, S_1 = 0.5 \text{ ¥}, S_2 = 1.0 \text{ ¥}$

$S_3 = 1.5 \text{ ¥}, S_4 = 2.0 \text{ ¥}$



Solution 2: Moor state graph

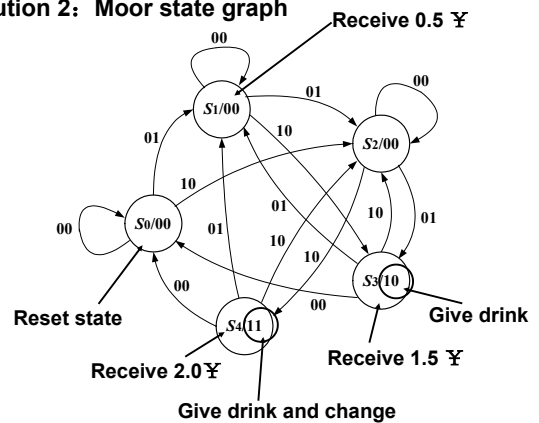

Moor state table

Present state	the next state			output Z_1Z_2
	$X_1X_2 = 00$	$X_1X_2 = 01$	$X_1X_2 = 10$	
S_0	S_0	S_1	S_2	00
S_1	S_1	S_2	S_3	00
S_2	S_2	S_3	S_4	00
S_3	S_0	S_1	S_2	10
S_4	S_0	S_1	S_2	11



Design a Sequential Lock with JK FF

- Inputs: X_1X_2 , Output: Z
States: R, B, C, E
- Input $00 \rightarrow 01 \rightarrow 11$ Sequentially from X_1X_2 state of the lock will be changed from **R** to **B** and then to **C**, and $Z=1$ (unlock)
- If the order is not above mentioned, state of the lock will be **E** (error)
- state of the lock will be reset to **R** whenever 00 are inputted from X_1X_2



1. Derivation of State Graphs and Tables

R—receive 00


B—receive 01 after 00,

C—receive 11 after 00, 01,

$Z=1$ (unlock)

E—error

X_1X_2	00	01	11	10	Z
R	R	B	E	E	0
B	R	E	C	E	0
C	R	E	E	E	1
E	R	E	E	E	0

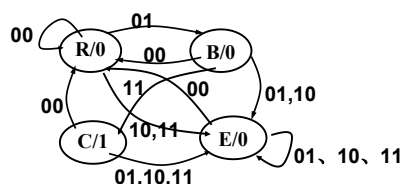

Design a Sequential Lock with JK FF

2. Reduction of State Table

3. State Assignment

R — 00, B — 01

C — 11, E — 10


$\therefore N=4, 2^2 = 4$

$\therefore k = 2$ flip flops

4. transition table



$X_1 \bar{X}_2$	$Y_1 Y_2$	$Y_1^{n+1} Y_2^{n+1}$	$J_1 \ K_1$	$J_2 \ K_2$	Z
0 0	0 0	0 0	0 ×	0 ×	0
0 0	0 1	0 0	0 ×	× 1	0
0 0	1 0	0 0	× 1	0 ×	0
0 0	1 1	0 0	× 1	× 1	1
0 1	0 0	0 1	0 ×	1 ×	0
0 1	0 1	1 0	1 ×	× 1	0
0 1	1 0	1 0	× 0	0 ×	0
0 1	1 1	1 0	× 0	× 1	1
1 0	0 0	1 0	1 ×	0 ×	0
1 0	0 1	1 0	1 ×	× 1	0
1 0	1 0	1 0	× 0	0 ×	0
1 0	1 1	1 0	× 0	× 1	1
1 1	0 0	1 0	1 ×	0 ×	0
1 1	0 1	1 1	1 ×	× 0	0
1 1	1 0	1 0	× 0	0 ×	0
1 1	1 1	1 0	× 0	× 1	1

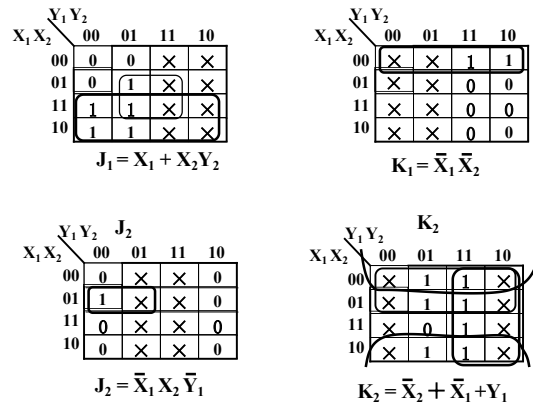



Design a Sequential Lock with JK FF

$X_1 \bar{X}_2$	$Y_1 Y_2$	J_1
00	00	1
01	00	1
11	00	1
10	00	1

$$Z = Y_1 Y_2$$

$$\begin{cases} J_1 = X_1 + X_2 Y_2 \\ K_1 = \bar{X}_1 \bar{X}_2 \\ J_2 = \bar{X}_1 X_2 \bar{Y}_1 \\ K_2 = \bar{X}_2 + \bar{X}_1 + Y_1 \\ Z = Y_1 Y_2 \end{cases}$$

5. Realize

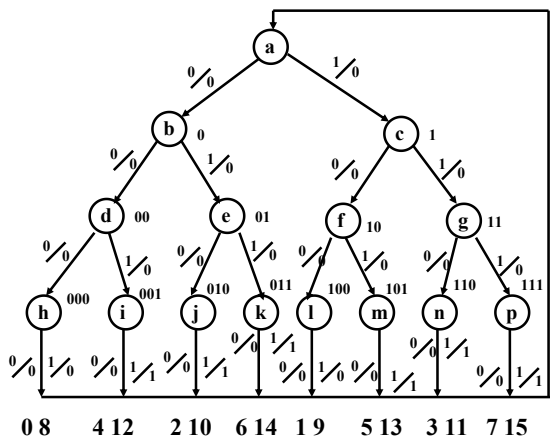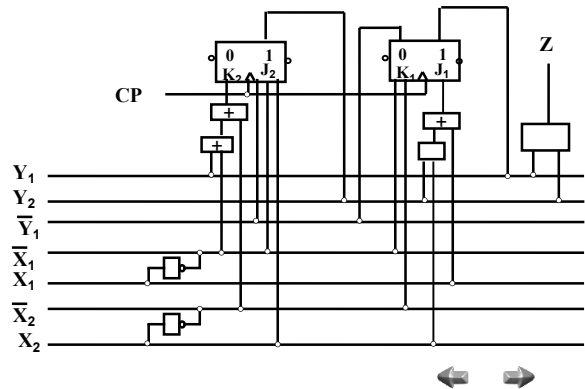

$Y_N \ X$	Y_{N+1}/Z		$Y_N \ X$	Y_{N+1}/Z	
	0	1		0	1
A	B/0	C/0	J	A/0	A/1
B	D/0	E/0	K	A/0	A/1
C	F/0	G/0	L	A/0	A/0
D	H/0	I/0	M	A/0	A/1
E	J/0	K/0	N	A/0	A/1
F	L/0	M/0	P	A/0	A/1
G	N/0	P/0			
H	A/0	A/0			
I	A/0	A/1			

X	0	1
A'	B'/0	B'/0
B'	C'/0	D'/0
C'	E'/0	F'/0
D'	F'/0	F'/0
E'	A'/0	A'/0
F'	A'/0	A'/1

State Assignment

Guideline 1: a given input, same next state, present state code should be adjacent

(C' D') (E' F')

Guideline 1: a given present state, it's next state code should be adjacent

(C' D') (E' F')

Guideline 3: Output same, present state code should be adjacent

(A' B' C' D' E')

Code Converter

② Reduction of State Table

Time	Input Sequence Received (Least Significant Bit First)	Present State	Next State		Present Output (Z)	
			X = 0	1	X = 0	1
t_0	reset	A	B	C	1	0
t_1	0	B	D	F	1	0
	1	C	E	G	0	1
t_2	00	D	H	L	0	1
	01	E	I	M	1	0
	10	F	J	N	1	0
	11	G	K	P	1	0
t_3	000	H	A	A	0	1
	001	I	A	A	0	1
	010	J	A	-	0	-
	011	K	A	-	0	-
	100	L	A	-	0	-
	101	M	A	-	1	-
	110	N	A	-	1	-
	111	P	A	-	1	-



Time	Present State	Next State		Present Output (Z)
		X = 0	1	
t_0	A	B	C	1 0
t_1	B	D	E	1 0
	C	E	E	0 1
t_2	D	H	H	0 1
	E	H	M	1 0
t_3	H	A	A	0 1
	M	A	-	1 -

Code Converter

④ Transition table

$Q_1 Q_2 Q_3$		$Q_1^+ Q_2^+ Q_3^+$		Z	
		X = 0	X = 1	X = 0	X = 1
A	000	100	101	1	0
B	100	111	110	1	0
C	101	110	110	0	1
D	111	011	011	0	1
E	110	011	010	1	0
H	011	000	000	0	1
M	010	000	x x x	1	x
-	001	x x x	x x x	x	x